

# Index

## A

- AC circuit analysis, steady-state AC circuit
  - complete solution for, 424–425, 429, 442–443
  - KVL, KCL and equivalent impedances, 423–424, 442–443
  - at single frequency, 429, 443–444
  - source transformation, 425–427, 443–444
  - superposition theorem, 429–430, 443–444
  - Thévenin and Norton equivalent circuits, 427–429, 443–444
- AC coupled, 408
- AC power
  - balanced three-phase systems
    - apparent power, 570
    - average power, 570
    - balanced delta-connected load, 572
    - balanced delta-connected source, 572–575
    - instantaneous power, 568–569
    - material consumption, 570–572
    - reactive power, 570
  - distribution
    - automotive alternator, 562
    - long-distance power transmission, neutral wire in, 565–567
    - neutral conductor, 558–559
    - phase voltages, 559–561
    - residential household, 563
    - single-phase three-wire power distribution system, 558–559
    - single-phase two-wire power distribution system, 558–559
    - split-phase distribution system, 558–559
    - synchronous three-phase AC generator, 562
    - synchronous three-phase AC motor, 562–563
    - three-phase four-wire power distribution system, 558–559
    - three-phase wye-wye circuit, 563–565
    - wye (Y) source and load configurations, 561
  - power factor correction
    - automatic power factor correction system, 554
    - capacitance value, 552
    - definition, 551
    - maximum power efficiency, principle of, 554–555
    - maximum power transfer, principle of, 556–557
    - power expressions, 553
  - types
    - apparent power, 545–547
    - arbitrary periodic AC signals, 541–542
    - average power, 545–547
    - instantaneous, 537
    - power angle, 543–544
    - power triangle, 547–549
    - reactive power, 545–547
    - resistor, capacitor, and inductor, average power for, 544–545
    - rms voltages and AC frequencies in world, 540–541
    - time-averaged, 538–540
    - wattmeter, 550
- AC voltage source, 19
- Aliasing frequency, 474
- Alternating-current circuits, 19–20
- Alternating current power supplies, 403
- American Telephone & Telegraph Company (AT&T), 454
- Ampere's law, 14–16, 595–596, 610
- Amplifier bandwidth, 467–468
- Amplifier circuit model, 207–209, 221, 254–255
  - amplifier DC imperfections and cancellation, 229, 261–263
    - input bias and offset currents, 231–232
    - input offset voltage, 229–230
    - output offset voltage, cancelling, 230–231
  - cascading amplifier stages, 227–229, 260–261
  - current flow in, 218–219
  - resistance values, choosing, 259
    - discrete resistance values and potentiometers, 222
    - gain tolerance, 222–223
    - non-inverting and inverting configurations, 221–222
  - virtual-ground circuit, 232–233
  - voltage amplifier vs. matched amplifier
    - input load bridging, 224–226
    - input load matching, 226–227

- Amplifier circuit model (*cont.*)
    - sensor's equivalent circuit and amplifier's equivalent circuit, 224
    - whole voltage amplifier circuit, model of, 223–224, 259–260
  - Amplifier DC imperfections
    - and cancellation, 229, 261–263
    - input bias and offset currents, 231–232
    - input offset voltage, 229–230
    - output offset voltage, cancelling, 230–231
  - Amplifier feedback loop, 211
  - Amplifier IC, 468–469
  - Amplifier operation, 256–257
    - amplifier circuit model, 207–209
    - ideal-amplifier model
      - concise form, operational amplifier in, 209
      - first summing-point constraint, 209–210
      - input/output resistances and output current, realistic values of, 210
    - open-circuit/open-loop voltage gain, 204
    - open-loop configuration, power rails and voltage transfer characteristic in, 205
    - operational amplifier comparator, 206–207
    - power rails, practice, 205–206
    - symbol and terminals, 203–204
  - Amplifier's equivalent circuit, 223
  - Amplitude, 403, 404, 408
    - transfer function, 452–453, 503
  - Analog filter, 447
  - Analog low-pass RC filter, 449
  - Analog-to-digital converter (ADC), 228, 241
  - Angle notation, 416
  - Angular frequency, 403
  - Antenna transmission, 171–172
  - Apparent power, 545–547, 570, 576
  - Arbitrary load, 576
  - Astable multivibrator, 342
  - Asymptotic expansion, 217
  - Automatic gain control, 222
  - Automatic power factor correction system, 554
  - Automatic traffic light, 524
  - Average power, 538–540, 545–547, 570, 576
- B**
- Balanced circuit, 565
  - Balanced delta-connected load, 572, 578
  - Balanced delta-connected source, 572–575, 578
  - Balanced phase voltages, 560
  - Balanced three-phase load, 561
  - Balun transformer, 613
  - Band-pass filter, 459, 514, 527
  - Band-reject filter, 514, 527
  - Band-stop, 515
  - Bandwidth of the series resonant RLC circuit, 502–505
  - Bell Telephone Company, 454
  - Binary counter, 220
  - Binary-weighted-input digital-to-analog converter, 219
  - Bipolar junction transistor (BJT), 20
  - Bistable amplifier circuit, 342–344
  - Blocking capacitor, 301, 315
  - Bode plots, 453–456, 505
  - Boundary element method, 11
  - Break frequency, 452
  - Buffer amplifier, 216–217, 347
  - Butterworth response, 513
  - Bypass capacitor*, 299–300, 315
- C**
- Capacitance, 19, 417
    - definitions, 273, 309
    - dynamic behavior, 290–292, 312–313
    - electric field energy, 274
    - electrostatic discharge, 275–276
    - 1- $\mu$ F Capacitor
      - blocking capacitor, 301, 315
      - capacitive touchscreens, 282–283
      - capacitor marking, 281–282
      - ceramic capacitor, 281
      - dielectric breakdown effect, 280
      - dielectric strength, 280
      - electrolytic capacitor, 281
      - normalized breakdown voltage, 280
      - relative permittivity, 280
      - tantalum capacitor, 281
    - finger capacitance, 282
    - to ground, 273–274, 309
    - in parallel and in series, 278–279
    - parallel-plate capacitor, 276–278
    - parasitic capacitance, 282
    - self-capacitance, 273, 309
    - of two conductors, 273
    - of two equal conductors, 274
  - Capacitance value, 552
  - Capacitive coupling, 221
  - Capacitive touchscreens
    - mutual-capacitance method, 283
    - self-capacitance method, 282–283
  - Capacitor voltage, continuity of, 325–326
  - Cascading amplifier stages, 227–229
  - Center frequency of the band-pass filter, 509
  - Channels, 408
  - Characteristic equation, 366–367
  - Charging, concept of, 337
  - Circuit analysis method, 167
  - Circuit current, 360
  - Circuits with resistances and capacitances, 349–351
  - Circuits with resistances and inductances, 351–353
  - Circuit with bypass capacitor, 355–357
  - Clamp on ammeter, 614
  - Clock frequency, 342
  - Clock signal, 342
  - Closed-loop AC gain, 465–467

- Closed-loop configuration, 204
  - Closed-loop DC gain, 465
  - Closed-loop gain, 214, 216, 242–243
  - Common-mode amplifier circuit gain, 236
  - Common-mode gain, 235–237
  - Common-mode input signal, 209
  - Common-mode rejection ratio (CMRR), 236
  - Common-mode voltage, 234
  - Comparator, 206–207, 344
  - Compensated Miller Integrator, 303–304, 316
  - Complementary solution, 356, 366
    - derivation of, 366–367
  - Complex conjugate, 544
  - Complex impedance, magnitude and phase of, 420–422
  - Complex power, 547, 576
  - Complex transfer function
    - high-pass filter, 457
    - low-pass filter, 457
    - next-stage filter load, 459–460
    - phase Bode plots, 458
  - Compliance, 19
  - Conductors, electrostatics, 7–8
    - charges, Coulomb force, and electric field, 3–4, 23–24
    - Coulomb's law, 9–10, 23–24
    - electric potential and electric voltage, 4–5, 23–24
    - electric voltage vs. ground, 5–7, 23–24
    - equipotential conductors, 7–8, 23–24
  - Conservative field, 5
  - Constant-speed water pump, 19
  - Constant-torque water pump, 18–19
  - Continuous and discrete Fourier transform
    - applications of, 476
    - bandlimited, 471, 473
    - definition of, 470, 474, 483
    - direct Fourier transform, 470
    - FFT, 473–474
    - Fourier spectrum, 470
    - Fry's Electronics store, 472
    - fundamental frequency, 473
    - of Gaussian pulse, 483
    - input pulse signal, 478–479
    - inverse DFT, 473–474
    - inverse Fourier transform, 470
    - mathematical properties of, 472–473
    - numerical differentiation, 476–478
    - properties of, 483
    - of rectangular pulse, 483
    - sampling points, 473, 483
    - sampling theorem, 475–476
    - sinc function, 471
    - structure of, 475
    - time-domain computational solution, 479–480
  - Contour integral, 5
  - Controls block diagram, 242
  - Core loss resistance, 616
  - Corner frequency, 455, 456
  - Coulomb force, 3–4
  - Coulomb's law, 9–10
  - Coupled inductors model, 640–641
    - conversion to T-network, 627–628
    - coupling coefficient, 628–630
    - mutual inductance(s), 627
    - N coupled inductors, 627
    - phasor form, 625–626
    - tuned radiators, 635–636
    - two coupled inductors, 624–625
    - two identical radiators, 634–635
    - wireless inductive power transfer, 630–634
  - Critical damping, 367
  - Cross product, 17
  - Current amplifier, 245, 246
  - Current divider circuit, 111–113, 135–136
  - Current flow
    - in amplifier circuit, 218–219
    - model, 11–13
  - Current limiter, 111, 135
  - Current source, 19
  - Current transformer, 614
  - Cutoff frequency, 508
- D**
- Damping coefficient, 360
  - Damping ratios, 367
    - solution behavior for, 368–369
  - 3-dB frequency, 455
  - 20-dB-per-decade roll-off, 455
  - DC coupled, 408
  - DC-coupled amplifiers, 220
  - DC-coupled single-supply amplifier, 232–233, 263
  - DC steady state, 18–19, 296
  - Decade, 455
  - Decoupling inductor, 301, 315
  - Dependent sources
    - arbitrary time-varying voltage, 64
    - current-controlled current source, 66
    - current-controlled voltage source, 66
    - definition, 64–65
    - Thévenin's theorem, 164–165
    - time-varying sources, 84–85
      - AC source polarity, 68
      - source amplitude, 67
    - transfer characteristics, 66–67, 84–85
    - voltage-controlled current source, 65–66
    - voltage-controlled voltage source, 65
  - Dependent vs. independent sources, 64, 84
  - Difference amplifier, 235–237, 264–265
    - differential gain and common-mode gain, 235–237, 264
    - differential input signal, 234–235
  - Differential amplifier circuit gain, 236
  - Differential gain, 235–237
  - Differential input signal, 209
  - Differential input voltage, 204
  - Differential-mode input resistance, 238
  - Differential sensor, 235
  - Differential voltage, 234

- Differentiator amplifier, 304–305
  - Digital memory cell, 329–330
  - Digital memory element, 344
  - Digital repeater, 206, 207
  - Digital signal processing (DSP), 476
  - Digital voltage, 206
  - Diode, 20
  - Direct current (DC), 13
  - Discrete cosine transform, 476
  - Discrete Fourier transform (DFT), 470, 483
    - bandlimited, 473
    - definition of, 474
    - FFT, 473–474
    - fundamental frequency, 473
    - inverse DFT, 473–474
    - sampling points, 473
    - structure of, 475
  - Discrete resistance values, 222
  - Dotted terminals, 594
  - Dual in-line (DIP-N) package, 203
  - Duality, 505–507
    - parallel connected second-order RLC circuit, 365
  - Duality of series/parallel RLC electric circuits, 365
  - Dynamic circuit elements
    - amplifier circuits, 302–303
    - blocking capacitor, 301, 315
    - bypass capacitor, 299–300, 315
    - Capacitance
      - dynamic behavior, 290–292, 312–313
      - electric field energy, 274
      - electrostatic discharge, 275–276, 309
      - 1- $\mu$ F capacitor, 281–283
      - finger capacitance, 282
      - to ground, 273–274
      - in parallel and in series, 278–279, 310
      - parallel-plate capacitor, 276–278, 309
      - parasitic capacitance, 282
      - self-capacitance, 273
      - of two conductors, 273
      - of two equal conductors, 274
    - compensated Miller Integrator, 303–304, 316
    - decoupling inductor, 301, 315
    - differentiator amplifier, 304–305
    - inductance
      - dynamic behavior, 293–295, 312–313
      - magnetic-field energy, 285
      - magnetic flux density, 284
      - 1-mH Inductor, 288–289
      - mutual inductance, 285
      - in parallel and in series, 287–288, 312
      - self-inductance, 284, 311
      - of solenoid, 285–287, 311–312
    - instantaneous energy and power, 295–296, 313
    - Miller integrator, 302–303, 315–316
    - steady state, 296–297, 314–315
    - at very high frequencies, 297–298
  - Dynamic process, 212–213
  - Dynamic random-access memory (DRAM), 329
  - Dynamic undershoot, 372
- E**
- Eddy current loss, 599
  - Electric circuits
    - conductors, electrostatics of
      - charges, Coulomb force, and electric field, 3–4, 23–24
      - Coulomb’s law, 9–10, 23–24
      - electric potential and electric voltage, 4–5, 23–24
      - electric voltage vs. ground, 5–7, 23–24
      - equipotential conductors, 7–8, 23–24
    - hydraulic and fluid mechanics analogies
      - for alternating-current circuits, 19–20, 25
      - in DC steady state, 18–19, 25
      - for semiconductor circuit components, 20, 25
    - steady-state current flow
      - current flow model and electrostatics, 11–13, 24–25
      - electric current, 11, 24–25
      - electric power transfer, origin of, 16–17
      - magnetostatics and Ampere’s law, 14–16
      - physical model of, 13–14, 24–25
  - Electric current density, 11
  - Electric field, 3–4
    - and electric potential, 7
  - Electric field intensity, 3
  - Electricity, 3
  - Electric load, 13
  - Electric permittivity, 9
  - Electric potential, 4–5
    - electric field and, 7
  - Electric power transfer, origin of, 16–17
  - Electric transformer, 19–20
    - autotransformer, 610–611
    - center-tapped transformer, 612–614
    - coupled inductors model
      - conversion to T-network, 627–628
      - coupling coefficient, 628–630
      - mutual inductance(s), 627
      - N coupled inductors, 627
      - phasor form, 625–626
      - tuned radiators, 635–636
      - two coupled inductors, 624–625
      - two identical radiators, 634–635
      - wireless inductive power transfer, 630–634
    - current transformer, 614–615
    - ideal transformer
      - AC power transfer, 591
      - Ampere’s law, 595–596
      - Faraday’s law of induction, 591–595
      - ideal loaded transformer, 596–598
      - magnetic circuit, 591
      - mechanical analogies of, 601
      - principally different, 591

- vs. real transformer, 598–600
  - transformer currents, appearance of, 595
- ideal transformer circuits
  - fixed load voltage, 607–608
  - fixed source voltage, 608–609
  - matching circuit, 605–607
  - phasor form, 602
  - referred/reflected load impedance, 604–605
  - referred/reflected source network, 602–604
- multiwinding transformer, 611–612
- real-transformer model
  - high-frequency transformer model, 622–623
  - model parameters and extraction, 616–618
  - nonideal low-frequency transformer, 616
  - nonideal transformer model, 618–621
  - transformer efficiency, 622
  - voltage regulation, 621–622
- Electric voltage, 4–5
  - vs. ground, 5–7
- Electromagnetic forming, 328–329
- Electromagnetic material processing, 324, 328–329
  - electromagnetic forming, 328–329
  - self-induced Lorentz force, 329
- Electromagnetic railgun, 326–328
- Electronic article surveillance (EAS), 518
- Electronic ignition system, 336, 340
- Electronic oscillators, 342
- Electrostatic discharge (ESD), 9, 275–276, 309
- Electrostatics of conductors, 3, 11–13
  - charges, Coulomb force, and electric field, 3–4, 23–24
  - Coulomb's law, 9–10, 23–24
  - electric potential and electric voltage, 4–5, 23–24
  - electric voltage vs. ground, 5–7, 23–24
  - equipotential conductors, 7–8, 23–24
- Energy-accumulating capacitor circuit, 330–332
- Energy-accumulating inductor circuit, 337–339
- Energy-release capacitor circuit, 322–324
- Energy-release inductor circuit, 333–336
- Energy-release RL circuit, 339–340
- Equipotential conductors, 7–8
- Equipotential lines, 6
- Equipotential surface, 6, 8, 12
- Equivalent circuit values, 618
- Equivalent impedances, 423–424
- Equivalent resistance, 103
- Error signal, 243–244
- Euler's formula, 409, 410
  
- F**
- Falling/trailing edge, 372
- Faraday's law, 520, 591–595
  - of induction, 59
- Fast Fourier transform (FFT), 473, 474, 483
- 1- $\mu$ F capacitor
  - capacitive touchscreens, 282–283
  - capacitor marking, 281–282
  - ceramic capacitor, 281
  - dielectric breakdown effect, 280
  - dielectric strength, 280
  - electrolytic capacitor, 281
  - normalized breakdown voltage, 280
  - relative permittivity, 280
  - tantalum capacitor, 281
- Feedback factor, 242
- Feedback gain, 242
- Feedback system
  - application of, 244–245
  - closed-loop gain and error signal, 242–244, 266–267
  - signal-flow diagram of, 242
  - voltage, current, transresistance, and transconductance amplifiers with negative feedback, 245–246, 267
- Field magnitude, 3
- Filter circuits
  - amplitude transfer function, 452–453
  - bode plot, 453–456
  - complex transfer function
    - high-pass filter, 457
    - low-pass filter, 457
    - next-stage filter load, 459–460
    - phase Bode plots, 458
  - continuous and discrete fourier transform
    - applications of, 476
    - bandlimited, 471, 473
    - definition of, 470, 474, 483
    - direct Fourier transform, 470
    - FFT, 473–474
    - Fourier spectrum, 470
    - Fry's Electronics store, 472
    - fundamental frequency, 473
    - of Gaussian pulse, 483
    - input pulse signal, 478–479
    - inverse DFT, 473–474
    - inverse Fourier transform, 470
    - mathematical properties of, 472–473
    - numerical differentiation, 476–478
    - properties of, 483
    - of rectangular pulse, 483
    - sampling points, 473, 483
    - sampling theorem, 475–476
    - sinc function, 471
    - structure of, 475
    - time-domain computational solution, 479–480
  - decibel, and roll-off, 453–456
- first-order filter circuits
  - analog filter, 447
  - analog low-pass RC filter, 449
  - DC circuit, 448
  - high-pass filter, 449, 451
  - load connected to filter, 451–452
  - MATLAB, 450–451
  - qualitative analysis, 448–449
  - RC voltage divider circuit, 447

- Filter circuits (*cont.*)
- real-valued voltages, 448
  - resistor voltage and capacitor voltage, 448
  - superposition principle, 450
  - two-port networks, 449
  - voltage division yields, 448
- half-power frequency, 452–453
- operational amplifier circuits
- amplifier bandwidth, 467–468
  - amplifier IC, 468–469
  - closed-loop AC gain, model of, 466–467
  - frequency bandwidth, 463
  - front-end amplifier, 463
  - open-loop AC gain, model of, 465–466
  - open-loop amplifier gain, 463–464
  - unity-gain bandwidth vs. gain-bandwidth product, 464–465
- phase transfer function, 456–457
- RL filter circuits, 460–462
- Filter operation, 478–479
- Filter termination resistance, 451
- First-order filter circuits
- analog filter, 447
  - analog low-pass RC filter, 449
  - DC circuit, 448
  - high-pass filter, 449, 451
  - load connected to filter, 451–452
  - MATLAB, 450–451
  - qualitative analysis, 448–449
  - RC voltage divider circuit, 447
  - real-valued voltages, 448
  - resistor voltage and capacitor voltage, 448
  - superposition principle, 450
  - two-port networks, 449
  - voltage division yields, 448
- First-order high-pass filter, 453, 481–482
- First-order low-pass filter, 453, 467, 481–482
- First-order ODE, 355
- First-order transient circuit, 358
- Flexible membrane, 19
- Fluid-flow analogy, 336, 337
- Fluid mechanics, 18
- Fluid mechanics analogies
- for alternating-current circuits, 19–20, 25
  - in DC steady state, 18–19, 25
  - for semiconductor circuit components, 20, 25
- Fluid mechanics analogy, 326, 336
- Fluid valves, 20
- Forced response, 356–357, 366
- Forcing function, 356, 362
- Forward/open-loop gain  $A$ , 242
- Fourier spectrum, 470, 484
- Frequency, 403, 408
- band, 455
  - response, 457
- Fry's Electronics store, 472
- G**
- Gain-bandwidth product, 464–465
- Gain tolerance, 222–223
- Gauss' theorem, 7
- Generator theorems, 188–195
- active linear networks, 154
  - circuit analysis method, 167
  - negative equivalent resistance, 165–166
  - short/open circuit methods, 154–155
  - solar panels, 155–156
  - source transformation theorem, 156–158
- Thévenin and Norton equivalents
- circuit solution, 163–164
  - dependent sources, 164–165
  - using Thévenin circuit solution, 161–163
  - without dependent sources
    - Norton's theorem, 159–161
    - Thévenin's theorem, 159
- Ground
- electric voltage vs., 5–7
  - reference, 5
- H**
- Half-power bandwidth, 503
- Half-power frequency, 452, 511, 513
- Harmonic voltage and current, phasors, steady-state AC circuit
- amplitude, frequency and phase measurements, 408
  - complex exponent, shorthand notation for, 416
  - harmonic voltage and current, 403–405
  - leading and lagging, 405–407
  - magnitude, 411–413
  - operations with phasor diagram, 413–416
  - phasor, definition of, 408–410
  - to real signals, 411
  - from real signals to, 410–411
- High-frequency asymptotes, 456
- High-frequency transformer model, 622–623
- High-pass filter (HPF), 449, 452–453, 527
- Homogeneous differential equation, 331
- Homogeneous second-order ODE, 353, 360
- Horseshoe coil, 525
- Horseshoe shape, 525
- Hydraulic analogies
- for alternating-current circuits, 19–20, 25
  - in DC steady state, 18–19, 25
  - for semiconductor circuit components, 20, 25
- Hysteresis loss, 599
- I**
- Ideal-amplifier model
- concise form, operational amplifier in, 209
  - first summing-point constraint, 209–210
  - input/output resistances and output current, realistic values of, 210

- Ideal filter, 508
  - Ideal magnetic core, 593
  - Ideal transformer
    - AC power transfer, 591
    - Ampere's law, 595–596
    - Faraday's law of induction, 591–595
    - ideal loaded transformer, 596–598
    - magnetic circuit, 591
    - mechanical analogies of, 601
    - principally different, 591
    - vs. real transformer, 598–600
    - transformer currents, appearance of, 595
  - Ideal-transformer model, 593, 637–639
  - Ideal voltmeter and ammeter, 85–87
    - absolute voltage, 72–73, 86–87
    - digital multimeter, 69
    - electric ground types, 71
    - fluid mechanics analogy, 70
    - ground and return current, 71–72
    - voltage drop, 72–73, 86–87
    - wrong connections, 69–70
  - Ideal wire, 14
  - Impedance, 339, 416
  - Impedance bridging, 224
  - Impedance matching, 557
  - Impedance of the capacitor, 421
  - Impedance of the inductor, 421
  - Impedance of the resistor, 420
  - Impedance phasor diagram, 421
  - Impedance, steady-state AC circuit, 339, 416, 419–422
    - concept of, 417–419, 439–442
    - of human body, 422
    - magnitude and phase of, 420–422
    - physical meaning of, 419–420, 439–442
  - Independent ideal voltage source, 80–82
    - active reference configuration, 52
    - electric circuit solution, 54
    - $v$ - $i$  characteristic, 52–53
    - polar device, 52
    - symbols, 53
    - voltage difference, 52
  - Independent sources
    - chemical battery, 83–84
      - battery voltage and capacity, 61
      - characteristics, 63
      - circuit model, 62–63
    - DC voltage generator, 59–60
    - ideal current source, 82
      - active reference configuration, 55–56
      - $v$ - $i$  characteristic, 56
      - symbols, 56–57
    - independent ideal voltage source, 80–82
      - active reference configuration, 52
      - electric circuit solution, 54
      - $v$ - $i$  characteristic, 52–53
      - polar device, 52
      - symbols, 53
    - voltage difference, 52
    - Norton's theorem, 159–161
    - practical current source, 57–58, 82–83
    - practical voltage source, 54–55, 80–82
    - Thévenin's theorem, 159
    - voltage source, 58–59
  - Inductance, 19, 417
    - dynamic behavior, 293–295, 312–313
    - magnetic-field energy, 285
    - magnetic flux density, 284
    - 1-mH Inductor, 288–289
    - mutual inductance, 285
    - in parallel and in series, 287–288
    - self-inductance, 284, 311
    - of solenoid, 285–287, 311–312
  - Inductively coupled system, 518
  - Inductor current, continuity of, 336–337
  - Inductor inertia, 336
  - Inhomogeneous first-order differential equation, 331
  - Inhomogeneous particular solution, 356
  - Input bias current, 231–232
  - Input load bridging, 224–226
  - Input load matching, 226–227
  - Input offset voltage, 204, 229–230
  - Input resistance of amplifier circuit, 207, 223–224
  - Input voltage to the amplifier circuit, 213
  - Instantaneous AC power, 537
  - Instrumentation amplifier, 265–266
    - building, 238
    - concept of, 238–240
    - in laboratory, 240–241
    - motivation for, 237–238
  - Integrated circuit (IC), 9, 203
  - Integration constants for second-order circuits, 368
  - Internal compensation, 463
  - Inverse fast Fourier transform (IFFT), 473, 474
  - Inverse Fourier transform, 470
  - Inverse stiffness, 19
  - Inverting amplifier, 215–216
  - Inverting input, 203
  - Inverting Schmitt trigger, 344
  - Iron loss, 599
- K**
- Kirchhoff's current law (KCL), 93–95, 127–128, 423–425
    - in phasor form, 425
  - Kirchhoff's voltage law (KVL), 14, 95–98, 128–129, 423–425
    - in phasor form, 425
- L**
- Laboratory ignition circuit, 340–341
  - Lagging, steady-state AC circuit, 405–407
  - Leading edge, 372
  - Leading, steady-state AC circuit, 405–407

- Leakage inductance, 616
- Light-emitting diodes (LEDs), 324
- Linear feedback system, 242
  - application of, 244–245
  - closed-loop gain and error signal, 242–244, 266–267
  - signal-flow diagram of, 242
  - voltage, current, transresistance, and transconductance amplifiers with negative feedback, 245–246, 267
- Linear functions, 349
- Linear oscillators, 342
- Linear passive circuit element
  - components, 31
  - elements, 31
  - resistance
    - current through resistance, 32–33
    - fixed resistors, 41–42
    - $v$ - $i$  characteristics, 34, 76–78
    - ohmic conductors, 36–39, 76–78
    - Ohm's law, 33
    - open and short circuits, 34–35
    - power delivered, 35–36, 78–79
    - power loss, 39–41, 78–79
    - symbols and terminals, 31
    - variable resistors, 42
    - voltage across resistance, 32
  - resistive sensors
    - circuit symbols, 45
    - photocell, 43–44
    - photoresistor, 44
    - physical component, 79
    - potentiometric position sensor, 44–45
    - sensitivity, 45
    - strain gauge, 44
    - thermistor, 43
    - thermocouple, 43–44
- Line currents, 565
- Line impedance, 567
- Line integral, 5
- Lines of force, 6–8
- Line-to-neutral voltages, 559
- Line voltages, 564–565
- LM148-series amplifiers, 466
- Load cell, 241
- Load line method, Nonlinear circuits, 198–200
  - with ideal diode, 177, 178
  - iterative method
    - explicit and implicit schemes, 178
    - inverse function, 178
    - for solar cell, 179–180
  - $v$ - $i$  characteristic, 176
- Load match, 547
- Load voltage, 357
- Load voltage amplitude, 537
- Loopstick antenna, 523
- Lorentz force, 59, 327
- Lower and upper half-power frequencies, 504
- Low-frequency asymptotes, 456
- Low-pass filter (LPF), 451, 452, 527
- Low-pass filter bandwidth, 511
- Low-resistance load, 452
- M**
- Magnetic circuit, 591
- Magnetic field, 14
- Magnetic-field intensity, 14
- Magnetic near-field calculations, 632
- Magnetizing current, 593
- Magnetizing inductance, 593
- Magnetostatics
  - and Ampere's law, 14–16
  - steady-state current flow and current flow model and electrostatics, 11–13, 24–25
  - electric current, 11, 24–25
  - physical model of, 13–14, 24–25
- Magnitude
  - of complex impedance, 420–422
  - phasors, 411–413
- Matched amplifier, amplifier circuit design
  - input load bridging, 224–226
  - input load matching, 226–227
  - sensor's equivalent circuit and amplifier's equivalent circuit, 224
- Matching transformer, 605–607
- Material conductivity, 11
- MATLAB script, 633
- Maximum amplitude, 501
- Maximum power transfer, 577
- Maxwell's minimum heat theorem, 98
- Mechanical analogy, 344, 359
- Mesh analysis, 187–188
  - linear circuits, 150–152
  - supermesh, 152–153
- Metal detector, 523
- Metal-oxide-semiconductor field-effect transistor, 20
- 1-mH Inductor, 288–289
- Miller integrator, 302–303, 315–316
- Multiple-input amplifier circuit, 219–220
- Multiple-input and multiple-output (MIMO) communication systems, 123
- N**
- Natural frequency, 367
- Natural response, 356–357, 366
- NC terminals. *see* Not connected terminals
- Near-field communication (NFC), 518
- Near-field communications
  - near-field wireless communication, 518
  - near-field wireless link, 522–523
  - receiver circuit, 520–521
  - transmitter circuit, 519–520
- Near-field wireless link, 518, 522–523
- Negative feedback
  - amplifier circuit, current flow in, 218–219, 258
  - amplifier feedback loop, 211



- dynamic process, 212–213
- idea of, 211
- mathematics, 217–218, 257–258
- multiple-input amplifier circuit, 219–220, 259
- summing-point constraints, 211
- two summing-point constraints, amplifier circuit
  - analysis using, 254–257
  - inverting amplifier, 215–216
  - non-inverting amplifier, 213–215
  - voltage follower/buffer amplifier, 216–217
- voltage, current, transresistance and transconductance amplifiers with, 245–246
- Networking theorems
  - arbitrary electric network, 98
  - electric network and topology, 127
    - branch currents and voltages, 94
    - branches, 91
    - loop, 92–93
    - mesh, 93
    - nodes, 92
    - series and parallel connections, 93
  - Kirchhoff's current law, 93–95, 127–128
  - Kirchhoff's voltage law, 95–98, 128–129
  - Maxwell's minimum heat theorem, 98
  - network ports, 99
  - Tellegen's theorem, 98, 99
- NMOS transistor, 20
- Nodal analysis, 145, 185–186
  - circuit simulators, 145
  - linear circuit
    - absolute node, 146
    - absolute values, 145
    - bridge circuit, 146
    - current source, 148–149
    - node voltages, 145
    - voltage source, 147
  - supernode, 149–150, 186–187
- Noise signals, 542
- Nonideal digital waveform
  - modeling circuit, 370–372
  - solution, 372–374
- Nonideal transformer model, 618–621
- Non-inverting amplifier, 213–215, 469
  - configuration, 467
- Non-inverting input, 203
- Non-inverting Schmitt trigger, 344
- Nonlinear circuits
  - load line method, 198–200
    - with ideal diode, 177, 178
  - iterative method, 178–180
  - $v$ - $i$  characteristic, 176
- Nonlinear passive circuit elements
  - dynamic resistance, 49–50
  - electronic switch, 50–51
  - equivalent resistance, 46
  - non-ohmic circuit elements, 47–48
    - ohmic element, 47
    - radiating monopole antenna, 46
    - saturation current, 48
    - Shockley equation, 48
    - static resistance, 48–49
- Non-ohmic circuit elements, 47–48
- Non-STC transient circuit, 353–354
- Nonzero phase, 405
- Norton theorem for steady-state AC circuits, 428
- Not connected (NC) terminals, 204
- Numerical differentiation, 476–478
- O**
- Octave, 455
- ODEs. *see* Ordinary differential equations
- Offset currents, 231–232
- Offset-null terminals, 230
- Ohmic conductor
  - average carrier velocity, 37–39
  - conductivities list, 38
  - total current, 36–37
- Ohm's law, 33, 218, 537, 544, 595
- Open-circuit transformer test, 618
- Open-circuit voltage gain, 204
- Open-loop AC amplifier gain, 465
- Open-loop amplifier gain, 463–464
- Open-loop configuration, 204
  - power rails and voltage transfer characteristic in, 205
- Open-loop gain behavior, 463–464
- Open-loop voltage gain, 204
- Operating at the same frequency, 427
- Operational amplifier circuits
  - amplifier bandwidth, 467–468
  - amplifier IC, 468–469
  - closed-loop AC gain, model of, 466–467
  - frequency bandwidth, 463
  - front-end amplifier, 463
  - open-loop AC gain, model of, 465–466
  - open-loop amplifier gain, 463–464
  - unity-gain bandwidth vs. gain-bandwidth product, 464–465
- Operational amplifier comparator, 206–207
- Ordinary differential equations (ODEs), 322
  - first-order, 355
  - homogeneous second-order, 353
  - second-order, 366
- Oscillation frequency, 346–347
- Oscilloscope, 405, 408
- Output offset voltage, canceling, 230–231
- Output resistance of amplifier circuit, 207, 223–224
- Output short-circuit current, 210
- Output terminal, 203
- Overdamping, 367
- Overshoot, 369–370

**P**

Parallel connected second-order RLC circuit  
 duality, 365  
 independent function, initial conditions  
 and choice of, 364  
 representation and qualitative operation, 363  
 voltage, circuit equation in terms, 363–364

Parallel resonant RLC circuit, 505–507

Parallel RLC circuit, 516–517

Parallel RLC tank circuit, 505

Particular solution, 356, 366

Passband, 455, 511

Passive linear circuit elements, 290

Passive reference configuration, 32–33

Peak-to-peak value, 405

Period, 404, 408

Phase, 403, 408  
 of complex impedance, 420–422

Phase transfer function, 456–457

Phase voltages, 559–561, 563–564

Phasors  
 current, 409  
 definition of, 408–410  
 diagram, 413–416  
 KVL and KCL on, 424–425  
 method, 521  
 shorthand notation, 416  
 steady-state AC circuit  
 amplitude, frequency and phase measurements,  
 408  
 complex exponent, shorthand notation for, 416  
 harmonic voltage and current, 403–405  
 leading and lagging, 405–407  
 magnitude, 411–413  
 operations with phasor diagram, 413–416  
 phasor, definition of, 408–410  
 to real signals, 411  
 from real signals to, 410–411  
 voltage, 409, 411, 417

Pk-Pk value, 405

Polar forms, 411–413

Positive feedback, 342  
 bistable amplifier circuit with, 342–344

Positive polarity, 594

Potential energy of a unit charge, 5

Potential transformers, 615

Potentiometers, 42, 222

Power amplifier, 224

Power angle, 543–544

Power conservation, 597

Power factor correction, 577

Power factor correction capacitor, 551

Power gain, 460

Power rails practice, 205–206

Power-related theorems, 129–130  
 Maxwell's minimum heat theorem, 98  
 Tellegen's theorem, 98, 99

Power terminal, 204

Power transfer, 195–198  
 maximum power theorem, 168–170  
 power efficiency, 170–171  
 solar panel, 172–175  
 transmitting antenna, 171–172

Power transfer function, 455

Power triangle, 547–549, 576

Poynting vector, 17

Primary winding, 592

Proximity sensors, 523–525

Pulse width modulation (PWM), 370

**Q**

Q-factor, 501

Quality factor of the nonideal inductor, 521

Quality factor of the series resonant RLC circuit, 500

Quasi-static magnetic dipole, 518

**R**

Radii of equivalent conductors, 571

Radio-frequency identification (RFID), 518, 630

Railgun, 326–328

Rails, 205

Rail-to-rail amplifiers, 206

RC circuits, 322  
 capacitor voltage, continuity of, 325–326, 379–381  
 digital memory cell, 329–330  
 electromagnetic material processing, 328–329, 381  
 electromagnetic railgun, 326–328, 381  
 energy-accumulating capacitor circuit, 330–332,  
 382–384  
 energy-release capacitor circuit, 322–324, 379–381  
 time constant of, 324–325, 379–381

RC voltage divider circuit, 447

Reactive power, 545–547, 570, 576

Realistic values, of input/output resistances and output  
 current, 210

Real-transformer model  
 high-frequency transformer model, 622–623  
 model parameters and extraction, 616–618  
 nonideal low-frequency transformer, 616  
 nonideal transformer model, 618–621  
 transformer efficiency, 622  
 voltage regulation, 621–622

Receiver circuit, 520–521

Rectangle rule, 473

Rectangular forms, 411–413

Reduction of resistive networks, 104–105

Relaxation constant, 323, 334

Relaxation oscillator, 342

Resistances, 417  
 and reactance, 546–547  
 in series and in parallel, 131–133  
 equivalent circuit element, 103–104

- parallel connection, 103
  - series connection, 102–103
  - Resistance values
    - amplifier circuit design, 259
    - discrete resistance values and potentiometers, 222
    - gain tolerance, 222–223
    - non-inverting and inverting configurations, 221–222
  - Resistive load, 576
  - Resistive sensors
    - circuit symbols, 45
    - photocell, 43–44
    - photoresistor, 44
    - potentiometric position sensor, 44–45
    - sensitivity, 45
    - strain gauge, 44
    - thermistor, 43
    - thermocouple, 43–44
  - Resonant circuit at the receiver (RX), 528
  - Resonant circuit at the transmitter (TX), 528
  - Resonant frequency, 499
  - Reversal property, 470, 473
  - Ringing in second-order circuits, 369
  - Rise time, 369–370
  - Rising edge, 372
  - RL circuits
    - energy-accumulating inductor circuit, 337–339, 386–387
    - energy-release inductor circuit, 333–336, 384–386
    - energy-release RL circuit with voltage supply, 339–340, 388
    - inductor current, continuity of, 336–337, 384–386
    - laboratory ignition circuit, 340–341, 388
  - RL filter circuits, 460–462
  - rms voltage and rms current, 538–539
  - Root-mean-square (rms), 539, 542
  
  - S**
  - Sampling interval, 473
  - Sampling theorem, 475, 484
  - Saturation mechanism, 342–343
  - Sawtooth/triangular wave, 542
  - Sawtooth wave, 542
  - Secondary winding, 593–594
  - Second-order band-pass RLC filter, 508–510
  - Second-order band-reject RLC filter, 514–516
  - Second-order high-pass RLC filter, 512–514
  - Second-order low-pass RLC filter, 511–512
  - Second-order ODE, 366
  - Second-order RLC circuits
    - construction of
      - band-pass and band-reject filters, 508
      - cutoff frequency, 508
      - ideal filter, 508
      - parallel RLC circuit, 516–517
      - second-order band-pass RLC filter, 508–510
      - second-order band-reject RLC filter, 514–516
      - second-order high-pass RLC filter, 512–514
      - second-order low-pass RLC filter, 511–512
    - near-field communications
      - near-field wireless communication, 518
      - near-field wireless link, 522–523
    - receiver circuit, 520–521
    - transmitter circuit, 519–520
  - proximity sensors, 523–525
  - theory of
    - self-oscillating ideal LC circuit, 495–497
    - series resonant ideal LC circuit, 497–498
    - series resonant RLC circuit (*see* Series resonant RLC circuit)
- Second-order transient circuits, 354
  - transient circuit fundamentals, 377–378
    - circuit current and capacitor voltage, initial conditions in, 361
    - independent function, step response and choice of, 362–363, 393–394
  - parallel connected second-order RLC circuit, 363–365, 394
  - series-connected second-order RLC circuit, 358–360, 393
  - types of, 358
- Second summing-point constraint, 211
- Self-capacitance, 9
- Self-induced Lorentz force, 329
- Self-oscillating LC circuit, 496
- Self-resonant, 524
- Semiconductor circuit components, 20
- Sending-end voltages, 607
- Sensitivity threshold, 225
- Sensor's equivalent circuit, 224
- Series and parallel network
  - capacitance, 278–279, 310
  - combined voltage and current dividers, 137–138
  - current divider circuit, 111–113, 135–136
  - current limiter, 111, 135
  - inductance, 287–288, 312
  - reduction of resistive networks, 104–105
  - resistances, 131–133
    - equivalent circuit element, 103–104
    - parallel connection, 103
    - series connection, 102–103
- sources, 130–131
  - combinations of current sources, 102
  - dual-polarity power supply, 101
  - parallel battery bank, 101–102
  - series-connected battery bank, 100–101
  - series vs parallel connection, 102
- voltage divider circuit, 133–134
  - as actuator circuit, 109–110, 134–135
  - KCL and KVL, 105
  - as sensor circuit, 107–109, 134–135
  - Wheatstone bridge, 113–114, 136–137
- Series-connected PFC capacitor, 555

- Series-connected second-order RLC circuit
  - circuit current, solution, 360
  - mechanical analogy, 359
  - representation and qualitative operation, 358–359
- Series resonant RLC circuit
  - bandwidth of, 502–505
  - duality, 505–507
  - quality factor of, 500–502
  - resonance condition, 498–500
- Series RLC circuit
  - complementary solution, derivation of, 366–367, 394–396
  - different damping ratios, solution behavior for, 368–369, 396
  - finding integration constants, 368, 396
  - nonideal digital waveform, 370–374
  - overshoot and rise time, 369–370, 396–397
  - second-order ODE, 366, 394–396
- Series RLC tank circuit, 500
- Short-circuit transformer test, 618
- Short/open circuit methods, 154–155
- Signal amplifier, 224
- Signal-flow diagram, 242
- Signals, 403
- sinc function, 471
- Single-ended sensors, 235
- Single input, 213
- Source circuit, 602
- Source frequency, 502
- Source impedances, 427, 567
- Sources in series and in parallel, 130–131
  - combinations of current sources, 102
  - dual-polarity power supply, 101
  - parallel battery bank, 101–102
  - series-connected battery bank, 100–101
  - series vs parallel connection, 102
- Source transformation, AC circuit analysis, 425–427
- Source transformation in the frequency domain, 425–426
- Source voltage, 427
- Spark gap radio, 341
- STC transient circuits, 376–377
  - circuits with resistances and capacitances, 349–351, 389–390
  - circuits with resistances and inductances, 351–353, 389–390
  - circuit with bypass capacitor, 355–357, 390–392
  - non-STC transient circuit, 353–354, 390
  - with two inductances and two resistances, 354, 355, 390
- Steady-state alternating current (AC) circuit, 403
  - AC circuit analysis
    - complete solution for, 424–425, 442–443
    - KVL, KCL and equivalent impedances, 423–424, 442–443
    - at single frequency, 429, 443–444
    - source transformation, 425–427, 443–444
    - superposition theorem, 429–430, 443–444
  - Thévenin and Norton equivalent circuits, 427–429, 443–444
- impedance
  - concept of, 417–419, 439–442
  - of human body, 422
  - magnitude and phase of, 420–422
  - physical meaning of, 419–420, 439–442
- phasors
  - amplitude, frequency and phase measurements, 408
  - complex exponent, shorthand notation for, 416
  - definition of, 408–410, 436–437
  - harmonic voltage and current, 403–405, 434–436
  - leading and lagging, 405–407, 434–436
  - magnitude, 411–413, 437–439
  - operations with phasor diagram, 413–416, 437–439
  - to real signals, 411, 436–437
  - from real signals to, 410–411, 436–437
- Steady-state current flow
  - electric power transfer, origin of, 16–17
  - and magnetostatics
    - current flow model and electrostatics, 11–13, 24–25
    - electric current, 11, 24–25
    - physical model of, 13–14, 24–25
    - magnetostatics and Ampere’s law, 14–16
- Steinmetz model, 616, 640
- Step-down transformer, 599
- Step-up transformer, 599
- Stopband, 455
- Stored magnetic-field energy, 598
- Summing amplifier, 219–220
- Summing/difference node, 242
- Summing point, 209
- Summing-point constraints, 211
- Superposition principle, 450, 565
- Superposition theorem, 138–141
  - for cellphone, 119–120
    - character, 123
  - independent sources, 116
  - linear circuit, 115
  - linearization procedure, 115
  - linear superposition, 116
  - for multifrequency AC circuits, 429–430
  - nonlinear circuit, 115–116
  - open circuit, 116
  - short circuit, 116
  - two-port networks, 122–123
  - voltage sources, 117, 118
- Y (wye) and  $\Delta$  (delta) networks, 140–141
  - balanced, 121–122, 140–141
  - conversions, 121
  - series/parallel equivalents, 120
  - three-terminal networks, 120
  - two-terminal networks, 120
- Surface charge density, 7

- Switching oscillators, 342
- Switching RC oscillator, 342, 345–346, 376, 389
- bistable amplifier circuit with the positive feedback, 342–344, 388–389
  - electronic oscillators, 342
  - oscillation frequency, 346–347, 389
  - 555 timer, 347–348
  - triggering, 344, 388–389
- T**
- Telephone hybrid circuit, 612
- Tellegen's theorem, 98, 99
- Thévenin and Norton equivalents
- circuit solution, 163–164
  - dependent sources, 164–165
  - using Them circuit solution, 161–163
- Thévenin equivalent method, 355–357, 502
- Thévenin impedance, 427
- Thévenin's theorem for steady-state AC circuits, 427
- Thévenin voltage, 427
- Three-phase balanced wye-wye circuit, 565
- Three-wire single-phase system, 613
- Threshold voltages, 344
- Time-averaged AC power, 538–540
- Time averaging, 537, 538
- Time constant, 323, 334, 349, 367
- of RC circuits, 324–325
- Time-domain computational solution, 478–479
- 555 timer, 347–348
- Timer integrated circuit (Timer IC), 348
- Time-varying sources, 84–85
- AC source polarity, 68
  - source amplitude, 67
- Total load impedance per phase, 567
- Trailing edge, 372
- Transconductance amplifiers, 245–246
- Transcranial magnetic stimulation (TMS), 479
- Transfer function multiplication, 484
- Transformer-based impedance matching, 640
- Transformer power efficiency, 622
- Transformer rating, 599–600
- Transient circuit fundamentals, 375
- RC circuits, 322
    - capacitor voltage, continuity of, 325–326, 379–381
    - digital memory cell, 329–330
    - electromagnetic material processing, 328–329, 381
    - electromagnetic railgun, 326–328, 381
    - energy-accumulating capacitor circuit, 330–332, 382–384
    - energy-release capacitor circuit, 322–324, 379–381
    - time constant of, 324–325, 379–381
  - RL circuits
    - energy-accumulating inductor circuit, 337–339, 386–387
    - energy-release inductor circuit, 333–336, 384–386
    - energy-release RL circuit with voltage supply, 339–340, 388
    - inductor current, continuity of, 336–337, 384–386
    - laboratory ignition circuit, 340–341, 388
    - second-order transient circuits, 377–378
      - circuit current and capacitor voltage, initial conditions in, 361
      - independent function, step response and choice of, 362–363, 393–394
      - parallel connected second-order RLC circuit, 363–365, 394
      - series-connected second-order RLC circuit, 358–360, 393
      - types of, 358
    - series RLC circuit
      - complementary solution, derivation of, 366–367, 394–396
      - different damping ratios, solution behavior for, 368–369, 396
      - finding integration constants, 368, 396
      - nonideal digital waveform, 370–374
      - overshoot and rise time, 369–370, 396–397
      - second-order ODE, 366, 394–396
  - STC transient circuits, 376–377
    - circuits with resistances and capacitances, 349–351, 389–390
    - circuits with resistances and inductances, 351–353, 389–390
    - circuit with bypass capacitor, 355–357, 390–392
    - non-STC transient circuit, 353–354, 390
    - with two inductances and two resistances, 354, 355, 390
  - switching RC oscillator, 342, 345–346, 376, 389
    - bistable amplifier circuit with the positive feedback, 342–344, 388–389
    - electronic oscillators, 342
    - oscillation frequency, 346–347, 389
    - 555 timer, 347–348
    - triggering, 344, 388–389
- Transmission line, 13
- Transmitter circuit, 519–520
- Transresistance, 245–246
- Transresistance amplifier, 66, 245
- Triangular wave, 542
- Triggering, 344, 388–389
- Trigger signal, 344
- Two independent parameters, 419
- Two-port networks, 449, 508
- Two summing-point constraints
- amplifier circuit analysis using, 254–257
    - inverting amplifier, 215–216
    - non-inverting amplifier, 213–215
    - voltage follower/buffer amplifier, 216–217
- Typical transformer circuit, 597
- U**
- Undamped resonant frequency, 360, 496
- Underdamping, 367
- Unity common-mode gain stage, 239
- Unity-gain bandwidth, 464–465

**V**

Variable-gain amplifier, 222  
Variac/variable AC transformer, 610  
Vector product, 17  
Virtual-ground circuit, 232–233  
Virtual-ground integrated circuits, 233  
Voltage amplifier, 224, 245  
    amplifier circuit design  
        input load bridging, 224–226  
        input load matching, 226–227  
        sensor's equivalent circuit and amplifier's  
            equivalent circuit, 224  
Voltage difference, 5  
Voltage divider circuit, 133–134  
    as actuator/circuit, 109–110, 134–135  
    KCL and KVL, 105  
    as sensor circuit, 107–109, 134–135  
Voltage divider rule, 106  
Voltage drop, 5  
Voltage follower/buffer amplifier, 216–217  
Voltage multiplication, 460  
Voltage multiplier, 522  
Voltage source, 18  
Volt-amperes (VA), 547  
Volumetric charge density, 7

**W**

Wattmeter, 550  
Well-designed transformer, 617  
Wheatstone bridge, 113–114, 136–137  
Whole voltage amplifier circuit model, 223–224  
Winding capacitances, 622  
Wireless communications, 17  
Wye-connected load, 561  
Wye-connected source, 561  
Wye-wye distribution system, 564  
Wye-wye power distribution system, 577–578

**Y**

Y (wye) and  $\Delta$  (delta) networks, 140–141  
    balanced, 121–122, 140–141  
    conversions, 121  
    series/parallel equivalents, 120  
    three-terminal networks, 120  
    two-terminal networks, 120

**Z**

Zero-level detector, 207