

Index

A

Adams-Bashforth-Moulton method
 approaches, 36–37
 Chen chaotic oscillator, 166, 168
 fractional-order chaotic oscillators, 163
 fractional-order derivative, 30
 FSM, 171
 general equation, linear multistep method,
 6, 7
 Grünwald-Letnikov, 165, 205
 Heart shape chaotic attractor, 14, 17
 Lorenz chaotic attractor, 10, 11
 Lü chaotic system, 166
 Lü-Chen chaotic attractor, 13, 15
 predictor-corrector, 33
 predictor stage, 169, 170
 RAM, 166
 ROM, 166
 Rössler chaotic attractor, 12, 13
 short memory (*see* Short memory principle)
 simulation, 36
 steps, 171, 172
 time domain numerical methods, 31
 VHDL description, 166
 Volterra's integral equation, 30
 V-shape chaotic system, 167
Anadigm Designer tool, 44, 47–54, 106, 108
Analog implementations
 amplifiers and fractors
 basic fractional-order differentiator and
 integrator, 96, 97
 circuit implementation, 95
 fractional-order integrator, 93
 fractional-order systems, 93
 Laplace domain, 96, 97

 Lorenz chaotic oscillator, 95
 pole and zero, 94
 FPAAs (*see* Field-programmable analog
 arrays (FPAAs))
 Lorenz chaotic circuit
 ladder fractance (*see* Ladder topology)
 tree fractance (*see* Tree topology)
Application-Specific Integrated Circuits
 (ASICs), 121
Arduino micro-controller, 3, 203
Arrays, memory design
 LUT, 149, 150
 RAM, 147, 148
 ROM, 148, 149
 shift register, 145, 146
Autonomous chaotic oscillators, 41
Autonomous system, 75

B

Bifurcation, 1
Binary truncation, 69
Biquad, 107, 111

C

Caputo fractional derivatives, 27–28
Chaos
 circuits and systems, 1–3
 control, 23, 24
 deterministic, 1
 generation, random numbers, 197–201
 mathematical definitions, 22
 secure communications, 23
Chaotic behavior, 2, 20, 82, 83, 86, 119, 121

- Chaotic masking, 191
- Chaotic oscillator
- Anadigm Designer software, simulation, 49–54
 - fixed-point, 69–73
 - FPAA (*see* Field-programmable analog arrays (FPAAs))
 - hardware implementation, 57
 - implementation, FPGAs (*see* Field-programmable gate arrays (FPGAs))
 - Lorenz, 42, 46
 - ODEs modeling, 41
 - three-dimensional autonomous system, 75
 - VHDL descriptions, 59–69
- Charef's approximation, 93
- Complementary-metal-oxide-semiconductor (CMOS), 41
- Computer arithmetic, 134, 135
- Configurable analog module (CAM), 46, 47, 49–52, 106, 107, 109–113
- Configurable logic blocks (CLBs), 59, 121, 204
- D**
- Deterministic chaos, 1
- Differential evolution (DE) algorithm, 84
- Digital-to-analog converter (DAC), 69, 70, 159
- E**
- Eigenvalue
- and equilibrium points, 3–4, 12
 - fractional-order chaotic oscillators, 76
 - imaginary and real parts, 77, 83
 - Jacobian matrix, 31
 - Lyapunov exponents, 20
 - OPCL synchronization technique, 181
- Electronic memories, *see* Arrays, memory design
- Embedded systems, 3, 16, 121, 203
- Entropy, 1, 3, 18–21, 204
- Equilibrium point
- classical nonlinear systems, 2–3
 - and eigenvalues, 3–4, 12
 - fractional-order chaotic oscillators, 76
 - fractional-order system, 31
 - and Jacobian matrix, 20, 77
- F**
- Field-programmable analog arrays (FPAAs)
- Anadigm QuadApex development board, 44
 - analog functions, 44, 204
 - analog implementations
 - algebraic operations, 110
 - Anadigm Designer 2 EDA tool, 110
 - biquad, 111
 - CAM configuration, 112, 113
 - EDA software, 106
 - ladder RC topology, 105, 108, 113
 - symbolic expression, 109
 - transfer function, 106
 - AN231E04 device, 46, 50, 51
 - CAM, 46–47
 - chaotic oscillators, 44, 46
 - configurable analog modules, 48
 - description, 44
 - implementation, Lorenz chaotic oscillator, 49
 - integrated differential amplifiers, 46
 - Lorenz equations, 45, 46
- Field-programmable gate arrays (FPGAs)
- Adams-Bashforth-Moulton (*see* Adams-Bashforth-Moulton method)
 - arrays memory (*see* Arrays, memory design)
 - Baboon image, 197
 - computer arithmetic (*see* Computer arithmetic)
 - correlations, 197
 - encryption operation, 196
 - engineering applications, 54
 - experimental attractors, 58, 59
 - fixed-point notation, 55
 - floating point representation, 205
 - fourth-order Runge-Kutta method, 58
 - grayscale/RGB type, 195
 - Grünwald-Letnikov (*see* Grünwald-Letnikov methods)
 - integer-order chaotic oscillators, 16
 - Lorenz chaotic oscillator, 58, 71
 - Lorenz system, 54
 - master-slave topology, 197
 - modern, 204
 - Runge-Kutta methods, 5–6
 - SCM blocks, 55–58
 - static memory, 59
 - synchronization, 196
 - time-domain numerical methods, 24
 - vendor designs, 59
 - VHDL description (*see* VHDL description)
- Fixed-point, 55, 69–73
- Forward Euler (FE)
- characteristics, 10
 - explicit method, 5
 - implicit numerical methods, 5
 - numerical integration methods, 5, 8

- Fractance
 - description, 95
 - fractional-order capacitor, 41
 - implementation, RC arrays, 95
 - ladder (*see* Ladder topology)
 - RC-circuit approximation, 97
 - tree (*see* Tree topology)
 - Fractional calculus, 22, 24, 115
 - Fractional integrator, 95
 - Fractional-order chaotic attractors
 - experiment observation
 - Chen chaotic oscillator, 157
 - Lorenz chaotic oscillator, 155, 159
 - Lü chaotic oscillator, 158
 - Rössler chaotic oscillator, 156
 - FPGA-based implementation, 154
 - Fractional-order chaotic master system, 183, 186, 188
 - Fractional-order chaotic oscillators
 - DE algorithm, 84
 - derivatives and integrals, 28
 - design parameters, 82
 - design variables, 76, 77
 - eigenvalue, 76, 83
 - equilibrium points, 76
 - fractional-order integrators, 41
 - frequency domain approximation, 93
 - Grünwald-Letnikov, 82
 - imaginary eigenvalues, 77
 - implementation (*see* Analog implementations)
 - integer-order system, 82
 - Jacobian matrix, 76, 77
 - nonlinear function, ladder type, 75, 76
 - numerical methods (*see* Numerical methods)
 - numerical simulation, 83
 - PSO algorithms (*see* Particle swarm optimization (PSO))
 - RAM and shift registers
 - operation, 152, 153
 - resource comparison, 151
 - Riemann–Liouville, 82
 - synchronization (*see* Synchronization)
 - Fractional-order chaotic systems
 - applications, 22
 - autonomous integer-order, 22
 - chaos, 22–23
 - electronic chaotic oscillator, 22
 - fractional calculus, 22
 - fractional derivatives, 24
 - fractional-order circuits, 22
 - master-slave synchronization techniques, 23
 - mechanical chaotic jerk model, 22
 - numerical methods, 23–24
 - theories, methods and applications, 23
 - theory of nonlinear oscillations, 22
 - Fractional-order derivatives and integrals
 - Caputo fractional derivatives, 27–28
 - fractional calculus, 24
 - fractional differintegral, 25
 - Grünwald-Letnikov, 25–26
 - Riemann-Liouville, 27
 - Fractional-order integrator
 - Charef’s approximation method, 93
 - description, 93
 - FPAA, 41
 - Laplace transfer function, 41
 - Fractional-order Lorenz’s chaotic oscillator, 75
 - Fractional-order systems, 23, 24, 31, 82, 93, 161, 162
 - Frequency domain approximation, 93, 100, 101
- G**
- Generator, 46, 85, 197–201, 203, 205
 - Gram–Schmidt orthonormalization, 79
 - Grünwald-Letnikov methods
 - approximations, 33, 82
 - Chen fractional-order chaotic oscillator, 124
 - FDE12 method, 34
 - FPGAs, 115–117 (*See also* Field-programmable gate arrays (FPGAs))
 - fractional differintegral, 25–26
 - fractional-order derivatives, 28, 29
 - Lorenz fractional-order chaotic oscillator, 122
 - Rössler fractional-order chaotic oscillator, 123
 - time domain, 30
 - time simulation, 99
- H**
- Hamiltonian forms
 - and OPCL (*see* Open-Plus-Closed-Loop (OPCL))
 - synchronization
 - chaotic oscillators, 176, 177
 - fractional-order Lorenz systems, 178, 179
 - fractional-order Rössler systems, 183–188
 - Hardware description language (HDL), 122

Hardware security, 204
 Hidden attractors, 1, 2, 23, 203, 204

I

Image encryption
 Baboon RGB, 193
 chaotic masking, 191
 correlations, 193, 194
 Lena RGB, 193
 master-slave topology, 192
 secure communication, 191, 192
 synchronization, 192

Integer-order chaotic oscillators
 Adams-Bashforth and Adams-Moulton, 6–7
 Forward Euler and Runge-Kutta, 5–6
 numerical methods, 4
 numerical simulation
 Chen's chaotic oscillator, 13
 Heart shape chaotic oscillator, 14, 17
 Lorenz chaotic oscillator, 10–12
 Rössler chaotic oscillator, 12, 13
 ODEs, 4–5
 one-step vs. multi-step numerical methods, 7–10

Integrated circuits, 203, 204
 Internet of Things (IoT), 203, 204

K

Kaplan–Yorke dimension (D_{KY}), 12, 18–21, 75, 81, 86–90

L

Ladder topology
 circuit theory, 100
 fractional-order integrator, 108, 113
 integer-order transfer functions, 99, 101
 nonlinear function, 75
 RC-circuit approximation, 97, 98
 series-connected resistor-capacitor arrays, 98

Laplace
 domain, 47, 96
 expressions, 98, 107
 transfer function, 41, 205

Lookup table (LUT), 149–151

Lorenz chaotic oscillator
 attractor and chaotic time series, 42
 FPGA-based implementation, 58

fractional-order, 95
 hardware implementation, 57
 opamp-based implementation, 42, 43

Lyapunov exponent
 chaotic behavior, 86
 chaotic time series data, 18
 coefficients, mathematical model, 18–19
 entropy, 18–19
 Kaplan–Yorke dimension, 19, 20, 86–90
 n -dimensional dynamical system, 19
 positive LE+ (*see* Positive Lyapunov exponent (LE+))
 TISEAN, 80–81
 values, 16
 Wolf's method (*see* Wolf's method)

M

Master-slave topology
 correlation, 175
 Hamiltonian forms, 176, 177
 OPCL, 177, 178
 secure communication, 175
 synchronization
 chaotic oscillators, 175
 fractional-order chaotic oscillators, 175, 176

Micro-controller, 3, 44, 203

MQTT protocol, 203

Multi-step methods
 Adams-Bashforth and Adams-Moulton, 6–7
 integer-order chaotic oscillators, 15
 Lorenz chaotic oscillator, 10

N

Nonlinear equations, 1
 Nonlinear system, 1

Numerical methods
 for fractional-order chaotic oscillators
 Adams-Bashforth-Moulton, 33
 derivatives and integrals, 28
 Grünwald-Letnikov, 31–32
 Riemann-Liouville, 28
 for integer-order chaotic oscillators
 Adams-Bashforth and Adams-Moulton, 6–7
 Forward Euler and Runge-Kutta, 5–6
 ODEs, 4–5
 one-step vs. multi-step numerical methods, 7–10

O

- Open-Plus-Closed-Loop (OPCL)
 - control systems combination, 177
 - fractional-order Lorenz systems, 179–183
 - fractional-order Rössler systems, 188–191
 - synchronization, 177, 178
- Operational amplifiers (opamps), 41–43, 95–97, 99
- Operational transconductance amplifiers (OTAs), 41
- Ordinary differential equations (ODE), 4–5, 7, 18–20, 41

P

- Particle swarm optimization (PSO), 21, 75, 76, 82–90
- Piecewise-linear (PWL), 1, 14
- Positive Lyapunov exponent (LE+), 20, 75
 - chaotic systems, 82
 - DE algorithm, 84, 85
 - and D_{KY} , 76, 83
 - evaluation, 79, 80
 - PSO algorithm, 86, 87

R

- Random access memories (RAMs), 147, 148, 151–153, 166, 169, 171, 204
- Random number, 72, 197–201, 203, 205
- Random number generators, 197–201
- Read only memories (ROMs), 148, 149, 151–153, 166, 169, 171
- Riemann-Liouville fractional differintegral, 27
- Runge-Kutta methods, 5–10, 12–17, 69

S

- Saturated nonlinear function (SNLF), 3
- Secure communication system, 191, 194–197, 199
- Short memory principle
 - ASICs, 121
 - behavior, binomial coefficients, 120
 - description, 119
 - Grünwald-Letnikov, 122–124 (*See also* Grünwald-Letnikov methods)
 - HDL, 122
 - simulations
 - fractional-order chaotic oscillator, 121
 - V-Shape fractional-order oscillator, 121, 128

- Simulation, fractional-order derivative
 - Adams-Bashforth-Moulton, 35–37
 - FDE12 predictor-corrector, 34, 35
 - Grünwald-Letnikov, 33–34
- Single constant multiplier (SCM), 55–58, 63–66
- Synchronization
 - FPGAs (*see* Field-programmable gate arrays (FPGAs))
 - Hamiltonian forms
 - Lorenz systems, 178, 179
 - Rössler systems, 178, 179
 - image encryption (*see* Image encryption)
 - master-slave (*see* Master-slave topology)
 - OPCL
 - Lorenz systems, 179–183
 - Rössler systems, 188–191
 - random number generator (*see* Random number generators)
- Synchronization chaotic oscillators, *see* Master-slave topology
- Synchronization error, 175, 178, 179, 182, 183, 185–189, 191, 196

T

- TISEAN (time series analysis), 80–81, 84–87
- Tree topology
 - circuits, 95
 - Grünwald-Letnikov method, 105
 - implementation, 104, 105
 - integer-order transfer functions, 99, 101
 - Lorenz chaotic circuit, 105
 - RC-circuit approximation, 97
 - values, 102, 104

V

- Very-high-speed-integrated-circuit hardware description language (VHDL), 60
- VHDL description
 - digital blocks
 - adder and subtractor, 136, 137
 - counter, 141, 142
 - cumulative summation block, 143–145
 - flip-flop, 142, 143
 - multiplexer, 139, 140
 - multiplier, 138, 139
 - FPGA, 54
 - fundamental units, 124

VHDL description (*cont.*)

hardware

architecture, 131–134

entity declaration, 130, 131

library package, 125–130

implementation, chaotic oscillators

ADDER block using 32 bit, 61

counter, 67

data type, 61

entity description, 61

Lorenz chaotic oscillator, 68–69

MULTIPLIER using 32 bit, 62–63

SCM block, 63–66

SUBTRACTOR using 32 bit, 62

logic and arithmetic, 59

VHDL programming, 54

W

Wolf's method, 18–20, 77–81, 83–87

evaluation, positive Lyapunov exponent,
79, 80

Gram–Schmidt orthonormalization, 79

Lyapunov exponent, calculation, 77, 79

main function, 79