

# Index

## 0–9

- 3 dB frequency
  - Butterworth filters, 39
  - Chebyshev filters, 59
- 3-OA biquads, 427

## A

- AGM, *see* arithmetic-geometric mean
- Akerberg-Mossberg biquad, 428
- All-pole functions, 389
- Allpass filter, 6
- Amplitude distortion, 4
- Approximating polynomial, 34
- Approximation, 15, 31, 34
  - all-pole, 89
    - Butterworth, 16, 34
    - Chebyshev, 16, 51
    - elliptic, 16, 143
    - inverse Chebyshev, 95
    - inverse Pascal, 112
    - Pascal, 16, 64
    - polynomial, 89
    - rational, 89
- Arithmetic-geometric mean, 147
  - calculation of elliptic integral, 147
  - calculation of elliptic sine, 147
  - definition, 147
- Attenuation, 1
  - effective, 227

## B

- Back-to-back connection, 319
- Band-elimination, *see* band-reject
- Band-reject, 10
  - bandwidth, 206
  - filter design, 185
- Bandpass filter design, 185
- Bandpass filters, 9
- Bandstop, *see* band-reject
- Bandwidth
  - band-reject filter, 10, 206
  - bandpass filter, 10, 197
- Biquadratic form, 389
- Biquads, 389
- Brune cycle, 479, 482
- Brune's method, 476
- Brune's theorem, 458

Bruton L.T., 328

Buffer, *see* voltage follower

- Butterworth, 34
  - 3 dB frequency, 39
  - approximation, 34
  - cut-off rate, 39
  - fractional order, 37
  - gain function, 35
  - integer order, 35
  - optimization, 37
  - order, 35
  - order equation, 37
  - passive filters, 250
  - prototype filters, 45
  - transfer function, 41

## C

- Canonic circuits, 27
- Canonical circuits, 257
- Cauer
  - realization, 489
  - synthesis I, 489
  - synthesis II, 490
- Cauer approximation, *see* elliptic approximation
- Center frequency
  - band-reject filter, 10
  - bandpass filter, 10
- Center frequency of BP filter, 197
- Center frequency of BR filter, 206
- Characteristic function, 230
- Chebyshev
  - 3 dB frequency, 59
  - cut-off rate, 60
  - decimal order, 55
  - even order passive, 270
  - integer order, 55
  - modified approximation, 274
  - optimization, 57
  - order equation, 55
  - passive filters, 266
  - polynomial, 51
  - prototype filters, 62
  - prototype transfer functions, 80
  - transfer function, 60
- Circuit order, 26
- Common-Mode Gain, 384
- Common-Mode Rejection Ratio, 384

Comparator, 384  
 Complete elliptic integral, 145  
     calculation, 147  
 Complex power, 220  
 Continued fraction property, 445  
 Conversion function, 422  
 Cross-cascade connection, 334  
 Current mirrors, 356  
 Cut-off frequency, 5  
 Cut-off rate  
     Butterworth, 39  
     Chebyshev, 60

**D**

Deboo integrator, 382  
 Decimal order  
     Butterworth, 36  
     Chebyshev, 55  
     elliptic, 158  
     Pascal, 73  
 Delay, 4  
 Delay equalizer, 402  
 Denormalization, 22  
 Differentiator, 367  
 Discrimination factor, 150  
 Distortion  
     amplitude, 4  
     group delay, 4  
     phase, 4

**E**

Effective attenuation, 227  
 Effective parameters, 226  
 Elliptic  
     even order passive, 309  
 Elliptic approximation, 143  
     design tables, 179  
     discrimination factor, 150  
     modified, 311  
     optimization, 159  
     order equation, 158  
     order nomograph, 177  
     passive filters, 302  
     poles and zeros, 164  
     transfer function, 164  
 Elliptic integral  
     complete, 145  
     non-complete, 146  
 Elliptic rational function, 149  
     definition, 149  
     poles and zeros, 149  
     properties, 150  
 Elliptic sine, 147  
     calculation, 147  
 ERF, *see* elliptic rational function  
 Even order  
     passive Chebyshev filters, 270  
     passive elliptic filters, 309  
     passive Pascal filters, 292

**F**

FDNR, 328  
 Feldtkeller's equation, 250, 290  
 Filter-appropriate Pascal polynomial, 67  
 Filters  
     active-RC, 12  
     continuous-time, 11  
     crystal, 12  
     current-mode, 12  
     discrete-time, 11  
     integrated, 12  
     mechanical, 12  
     microwave, 12  
     passive, 12  
     prototype, 24  
     sampled-data, 11  
     switched capacitor, 12  
 Floating inductor, 319  
 Foster method, 487  
 Fractional order  
     Butterworth, 37  
     Chebyshev, 55  
     elliptic, 158  
 Frequency dependent impedance scaling, 328  
 Frequency response  
     magnitude, 1  
     phase, 1  
 Frequency transformations, 185  
     lowpass to band-reject, 206  
     lowpass to bandpass, 197  
     lowpass to highpass, 185  
     RC-CR, 189

**G**

Gain  
     function, 1  
     logarithmic, 1  
     plain, 1  
     plots, 2  
 Group delay, 4

**H**

Highpass  
     filter design, 185  
     filters, 9  
     notch, 401  
     transformation, 185  
 Hurwitz  
     continued fraction property, 445  
     polynomial, 445, 448  
     polynomial (strictly), 448  
 Hurwitz test, 449

**I**

Ideal filter  
     allpass, 6  
     band-reject, 5  
     bandpass, 5  
     highpass, 5  
     lowpass, 5  
     impulse response, 5

- Ideal transmission, 4
- Immittance function, 458
- Impedance matching, 223
- Insertion parameters, *see* effective parameters
- Integer order
  - Butterworth, 35
  - Chebyshev, 55
  - Pascal, 73
- Integrator, 376
  - Deboo, 382
  - inverting, 365, 377
  - loss, 367
  - lossy, 365
  - Miller, 365
  - non-inverting, 380
- Inverse Chebyshev approximation, 95
- Inverse Pascal approximation, 112
  - definition, 119
  - design, 121
  - design tables, 132
  - order, 122
  - transfer function, 126
- Inverting voltage amplifier, 361
- J**
- Jacobi elliptic sine, 147
- K**
- KHN circuit, 430
- L**
- Ladder filters, 13
- Lattice filters, 13
- LC circuits, 485
- LC functions, 485
- LC synthesis, 485
- Leap-frog filters, 341
- Linear Transformation Active Filters, 331
  - cross-cascade connection, 334
  - input termination, 335
  - output termination, 336
  - transformation matrix, 332
- Load, 6
- Logarithmic gain, 1
- Lossy integrator, 365
- Lowpass filters, 7
- Lowpass to band-reject transformation, 206
- Lowpass to bandpass transformation, 197
- Lowpass to highpass transformation, 185
- Lowpass-notch, 401
- LP-BP transformation, 197
- LP-BR transformation, 206
- LP-HP transformation, 185
- LTA, *see* Linear Transformation Active Filters
- M**
- Matching, *see* impedance matching
- Maximally flat, 36
- Maximum power transfer theorem, 223
- Minimum positive real, 473, 476
- Modified Chebyshev approximation, 274
- Modified Pascal approximation, 300
- Modified transmission matrix, 331
- N**
- Natural frequencies, 389
- Negative impedance converter, 374
- NIC, *see* negative impedance converter
- Nome, 147
- Normalization, 14, 19, 21
- Notch, *see* band-reject, 400
- Notch-highpass, 401
- Notch-lowpass, 401
- O**
- OA, *see* op amp
- One-pole model, 354
- Op amp
  - CMG, 384
  - CMRR, 384
  - current-mode, 355
  - imperfections, 382
  - integrator model, 355
  - one-pole model, 354
  - open-loop bandwidth, 354
  - open-loop gain, 350
  - slew rate, 383
  - voltage-mode, 350
- Open-loop bandwidth, 354
- Operational amplifier, *see* op amp
- Order equation
  - Butterworth, 37
  - Chebyshev, 55
  - elliptic approximation, 158
- Order of circuit, 26, 389
- P**
- Partial fractions, 457
- Pascal
  - approximation, 64
  - even order passive filters, 292
  - modified approximation, 300
  - optimization, 71
  - order calculation, 73
  - order nomograph, 73
  - passive filters, 286
  - polynomial, 67
  - transfer function, 73
- Passband, 7
- Passive filters
  - Butterworth, 250
  - Chebyshev, 266
  - elliptic, 302
  - Pascal, 286
- Phase distortion, 4
- Phase equalizer, 402
- Phase response, 1
- Plain gain, 1
- Pole removals, 465
  - constant, 472
  - imaginary pole pair at  $s = \pm j\omega_1$ , 469

- Pole removals (*cont.*)
  - partial removal, 471
  - pole at  $s = 0$ , 465
  - pole at  $s = \infty$ , 468
- Pole residue, 457
- Pole-zero diagram, 449
- Polynomial, 441
  - degree, 441
  - even part, 444
  - Hurwitz, 445
  - odd part, 444
  - remainder theorem, 443
  - roots, 441
  - strictly Hurwitz, 445, 448
- Positive real
  - definition I, 458
  - definition II, 459
  - definition III, 460
  - function, 458
  - property, 458
- Power
  - apparent, 220
  - average, 220
  - complex, 220
  - factor, 220
  - maximum transfer, 223
  - reactive, 220
  - real, 220
  - reflected, 229
- Precise filter design method, 219
- Prototype cutoff frequency, 393
- Prototype filters, 24
  - Butterworth, 45
  - Chebyshev, 62
- Q**
- Quality factor, 389
- R**
- Rational approximations, 89
  - definition, 89
  - elliptic, 143
  - inverse Chebyshev, 95
  - inverse Pascal, 112
- Rational functions, 449
- RC-CR transformation, 189
- Reactance, 486
- Realizable
  - band-reject filter, 10
  - bandpass filter, 9
  - highpass filter, 9
  - lowpass filter, 7
- Reflected power, 229, 230
- Reflection coefficient, 229, 230
- Reflectionless impedance matching, 223
- Remainder function, 465
- Remainder theorem, 443
- Residue, *see* pole residue
- Routh criterion, 448
- Routh test, 449
- S**
- SAB, 405
- Scaling, 14, 19
  - frequency, 14, 20
  - impedance, 14, 19
  - normalization, 14
- Second order functions, 391
- Second order LP functions, 391
- Selectivity, 7
- Simulated inductor, 316
  - a general approach, 321
  - Antoniou's, 318
  - floating, 319
  - grounded, 317, 319, 325
  - Riordan's, 316
- Simulation of
  - inductors, 316
  - ladder filters, 315
- Single amplifier biquads, 405
- Slew rate, 383
- Source, 6
- State variable filter, 430
- Stopband, 7
- Stopband edge frequency, 8
- Strictly Hurwitz polynomial, 445, 448
- Sturm's theorem, 451
- Su Kendal L., 179
- Subtractor, 367
- Supercapacitor, *see* FDNR
- Susceptance, 486
- T**
- Theta functions, 148
- Tow-Thomas, 427
- Transfer function, 1, 6
- Transimpedance, 357
- Transmission
  - distortionless, 5
  - ideal, 4, 5
  - without distortion, 4
- Transmission function, 6, 230
- Transmission parameters, *see* effective parameters
- Transmission zeros, 1, 89
- U**
- Universal filter, 431
- V**
- Voltage follower, 360
- W**
- WAF, *see* Wave active filters
- Wave active filters, 340
- Z**
- Zero shifting, 471